

Computer Architecture

Lecture 1

Course Information

- Course Name: Computer Architecture
- Course Code: EE2013
- Semester: Spring 2026
- Prerequisites: Computer Organization and Assembly Language (EE2003)

Textbook and References

Text Books:

- David A. Patterson, John L. Hennessy, Computer Organization and Design: The hardware/software interface, RISC-V Edition.
- David A. Patterson, John L. Hennessy, Computer Architecture: A Quantitative Approach 6th edition.

Reference books:

- John Paul Shen and Mikko H. Lipasti Modern Processor Design: Fundamentals of Superscalar Processors.
- M. Morris Mano, Computer System Architecture 3rd Edition 1993, Prentice Hall.
- William Stallings, Computer Organization and Architecture: Designing for Performance, Prentice Hall, 11th edition.

Course Objectives


- The main objective of this course is to provide a profound understanding of the architectural design and internal working of a microprocessor, enabling computer science students to appreciate concepts like optimization and hardware level performance issues. This course also introduces advanced concepts including pipelining and superscalar architecture. Additionally, the fundamentals of GPUs are discussed.

Grading

- | | |
|------------------|-----|
| • Quizzes | 15% |
| • Assignments | 10% |
| • 2 Midterm Exam | 30% |
| • Final Exam | 45% |

**Constructing a basic Arithmetic
Logic Unit
(Textbook 1, Appendix A.5)**

1-bit logical unit for AND and OR.

 

Review: 2's Complement Binary Representation

	2'sc binary	decimal
$-2^3 =$	1000	-8
$-(2^3 - 1) =$	1001	-7
	1010	-6
	1011	-5
	1100	-4
	1101	-3
	1110	-2
	1111	-1
	0000	0
	0001	1
	0010	2
	0011	3
	0100	4
	0101	5
	0110	6
	0111	7

1011


and add a 1

1010

complement all the bits

$2^3 - 1 =$

Binary Addition

 


Overflow Detection

- ❑ Overflow: the result is too large to represent in 32 bits
- ❑ Overflow occurs when
 - adding two positives yields a negative
 - or, adding two negatives gives a positive
 - or, subtract a negative from a positive gives a negative
 - or, subtract a positive from a negative gives a positive
- ❑ On your own: **Prove** you can detect overflow by:
 - Carry *into* MSB xor Carry *out of* MSB, ex for 4 bit signed numbers

	0	1	1	1		7
		0	1	1	1	
+		0	0	1	1	3
	1	0	1	0		-6

	1	0	1	0		-4
		1	1	0	0	
+		1	0	1	1	-5
	0	1	1	1		7

A 1-bit Adder

 

A	B	carry_in	carry_out	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)$$


$$\text{Sum} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$

- ❑ How can we use it to build a 64-bit adder?
- ❑ How can we modify it easily to build an adder/subtractor?


Adder hardware for CarryOut signal

Inputs		
a	b	CarryIn
0	1	1
1	0	1
1	1	0
1	1	1

 □ $\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)$




 A 1-bit ALU that performs AND, OR, and addition




Function	Operation
and	00
or	01
add	10

A 64-bit ALU

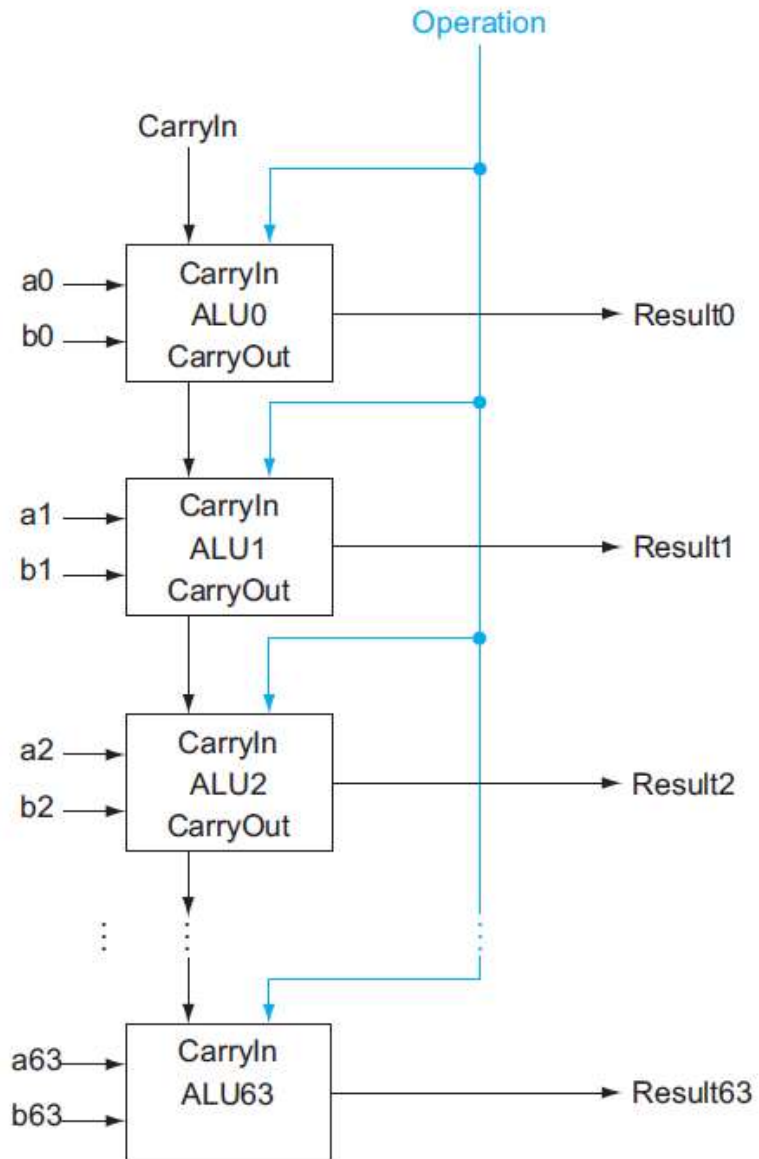


A 1-bit ALU that performs AND, OR, and addition on a and b or a and b-invert (for subtraction)


Function	Binvert	CarryIn	Operation
and	0	0	00
or	0	0	01
add	0	0	10
sub	1	1	10

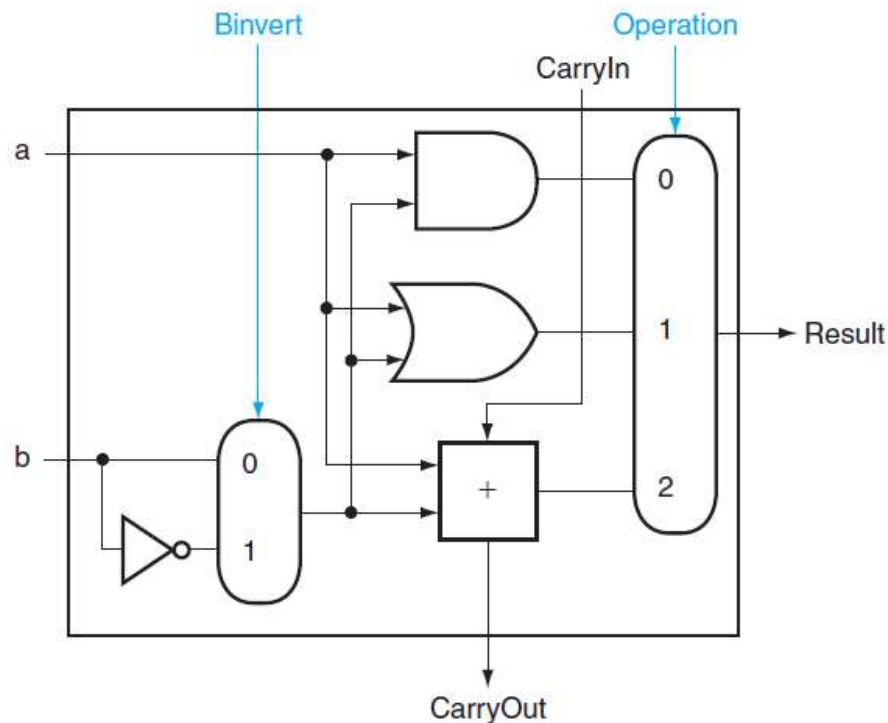

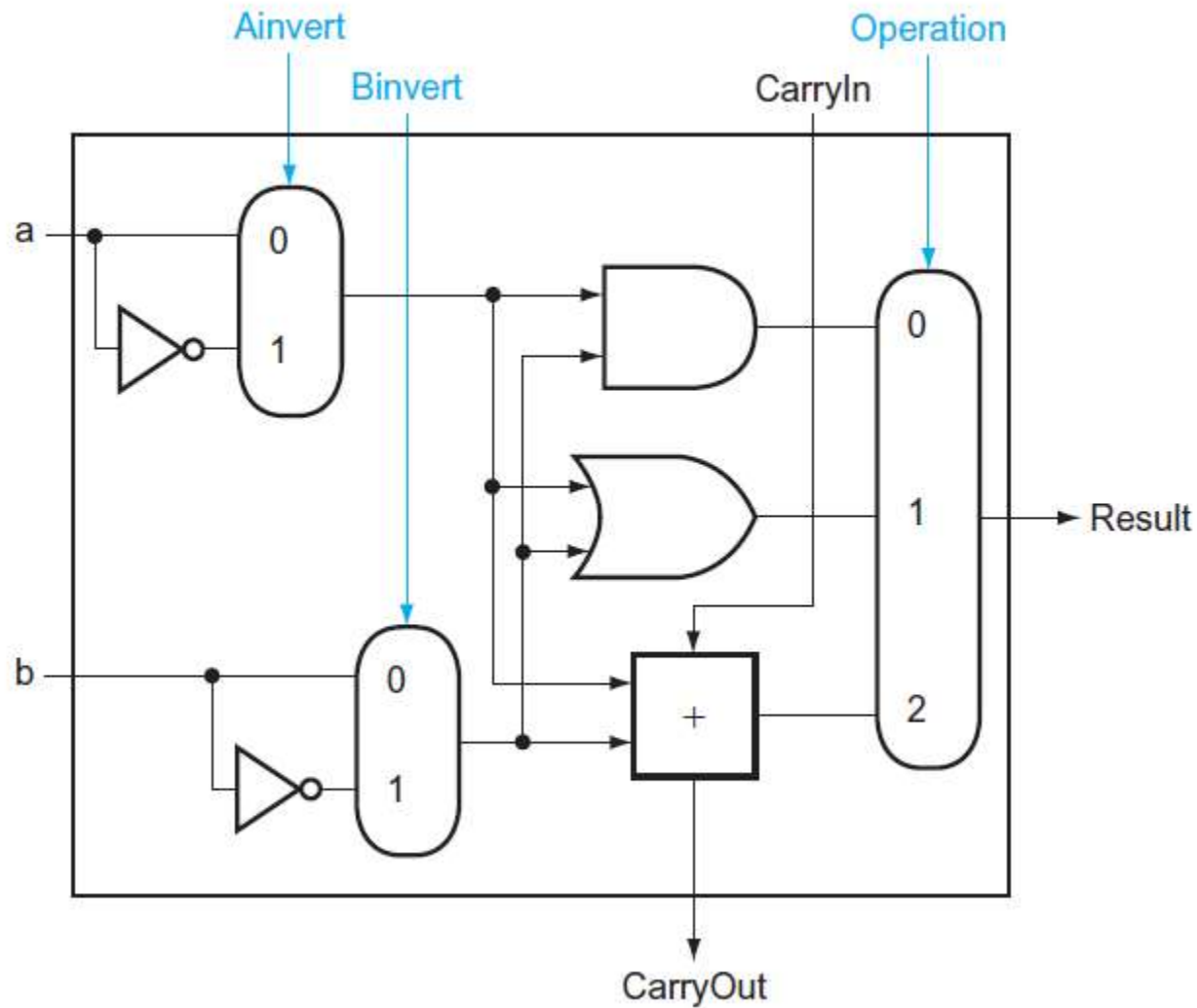A 1-bit ALU that performs AND, OR, and addition on a and b or a-invert and b-invert.




Adding slt operation

 


Function	Binvert	Operation
and	0	00
or	0	01
add	0	10
sub	1	10
slt	1	11

ALU

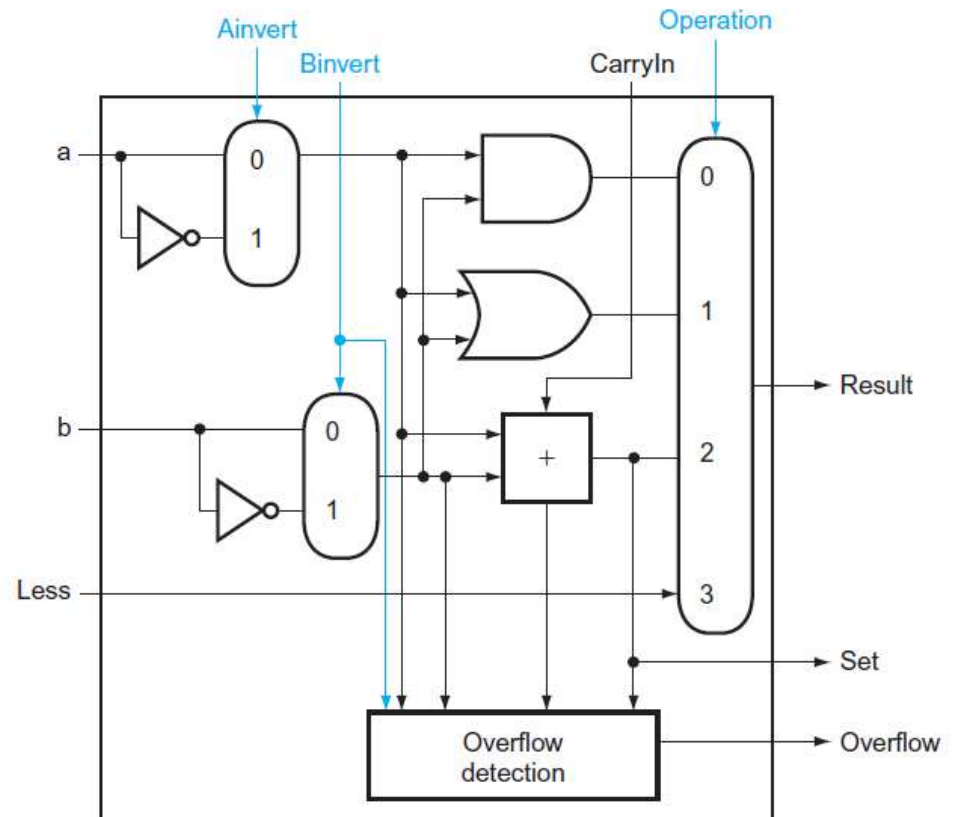

Function	Bnegate	Operation
and	0	00
or	0	01
add	0	10
sub	1	10
slt	1	11

ALU

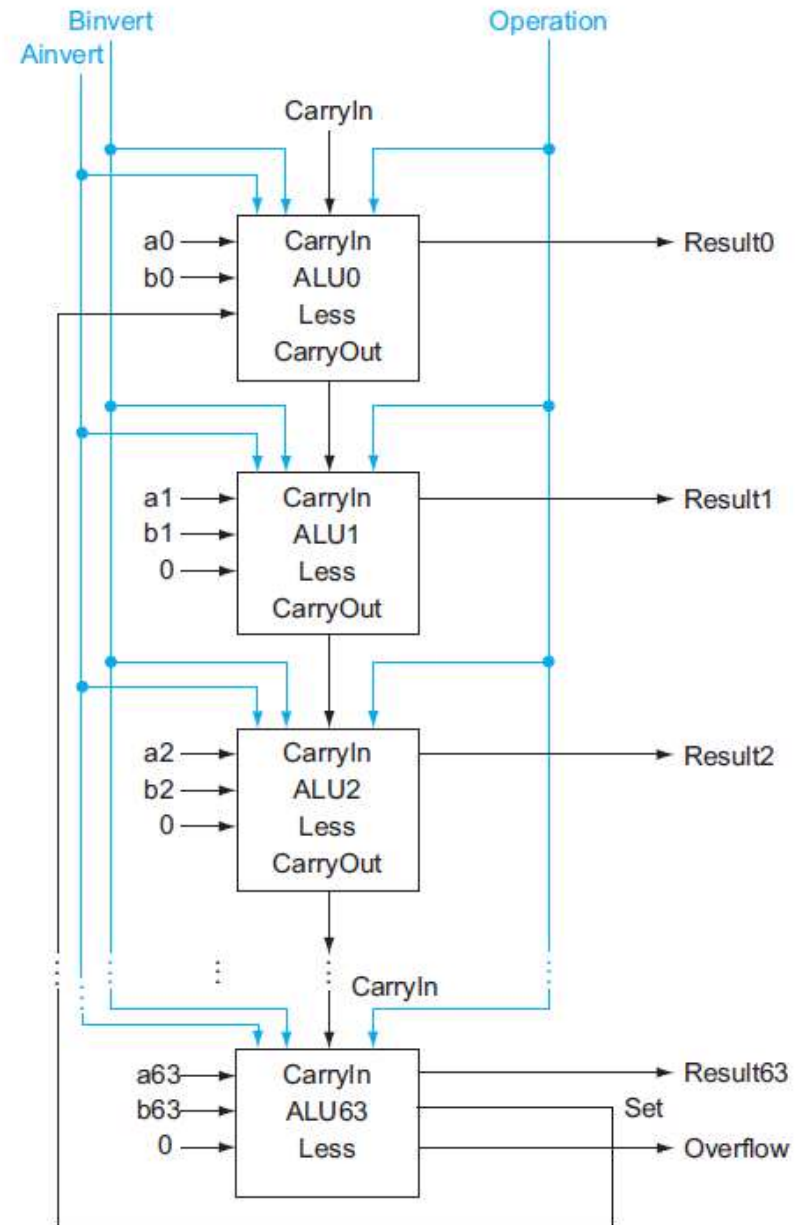

ALU with a zero detector

